

VLSI Design

Dadda Multiplier 8×8

EE 671 : Assignment #4

Simranjeet Singh - 183076005

November 12, 2018

Dadda Reduction

Dadda Multiplier 8×8 reduction is shown in the following Figure 1. Table represent the number of half adder and full adder required to implement this multiplier.

Table 1: Number of adder


Adder	Number
Full Adder	48
Half Adder	8

Given delay

As per the given in the Assignment problem statement.

Table 2: Delay parameter

Adder	Sum Delay	Carry Delay
Full Adder	120 ps	80 ps
Half Adder	70 ps	40 ps
MUX	—	50 ps

 

Simulation Result

Result Shown in the below figure is tested by applying the input $(FF \times FF) + 0F0F = 10D10$. The complete result is available at 810 ps

Observation

I have tested the code on different test vector to check the delay model. The worst delay i was finding on the following case:

$(FF \times 0F) + 00FF = 00F0$ - 910 ps

 


Figure 2: Dadda Multiplier Simulation