

# VLSI Design

## 32-Bit Brent-Kung Adder EE 671 : Assignment #3

Simranjeet Singh - 183076005


October 21, 2018

### Basic Components


This section includes all the basic components required for 32-bit Brent-Kung adder. All the components are designed and simulated for SCL's 180 nm process.

#### Minimum Sized Inverter

Design and Layout

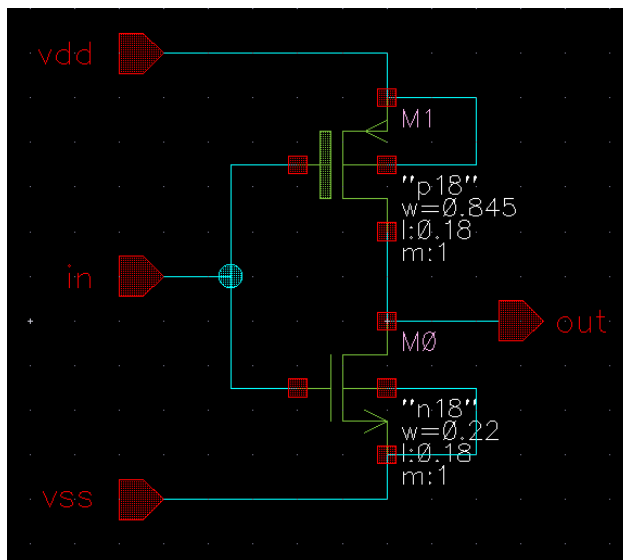

(a) Schematic

 

(b) Layout

Figure 1: Minimum Sized Inverter


Inverter Parameter  $\gamma \left( \frac{W_p}{W_n} \right)$  is chosen to get nearly equal rise time and fall time under Typical-Typical process corner (SCL).

Table 1: Design


Parameter	Value
P-MOS Gate Width $W_p$	$0.85 \mu m$
P-MOS Gate Length $L_p$	$0.18 \mu m$
N-MOS Gate Width $W_n$	$0.22 \mu m$
N-MOS Gate Length $L_n$	$0.81 \mu m$

## Generate using Domino logic

### Design and Layout

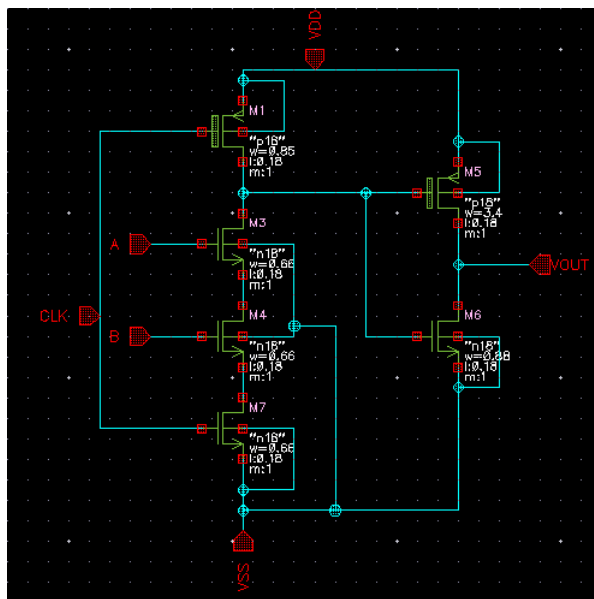

(a) Schematic

 


(b) Layout


Figure 2: Generate using domino logic

## Propagate using Domino logic

### Design and Layout

 

(a) Schematic

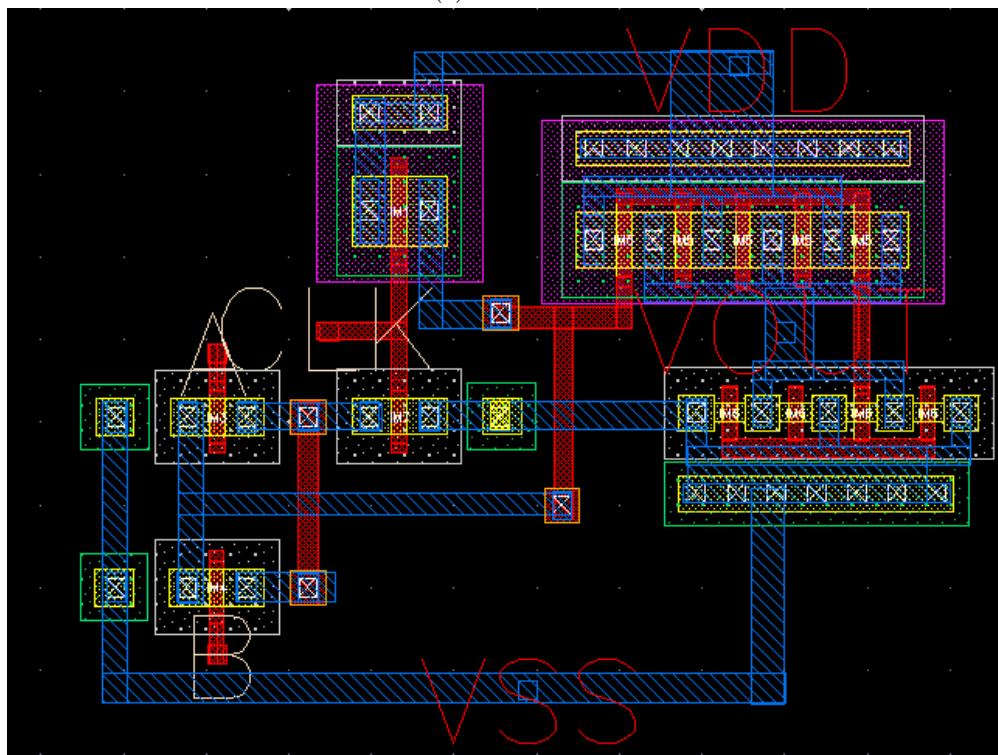


(b) Layout


Figure 3: Propagate using domino logic

## Carry Generator

### Design and Layout

 


(a) Schematic

 


(b) Layout

Figure 4: Carry Generator

## LVS and PEX generation

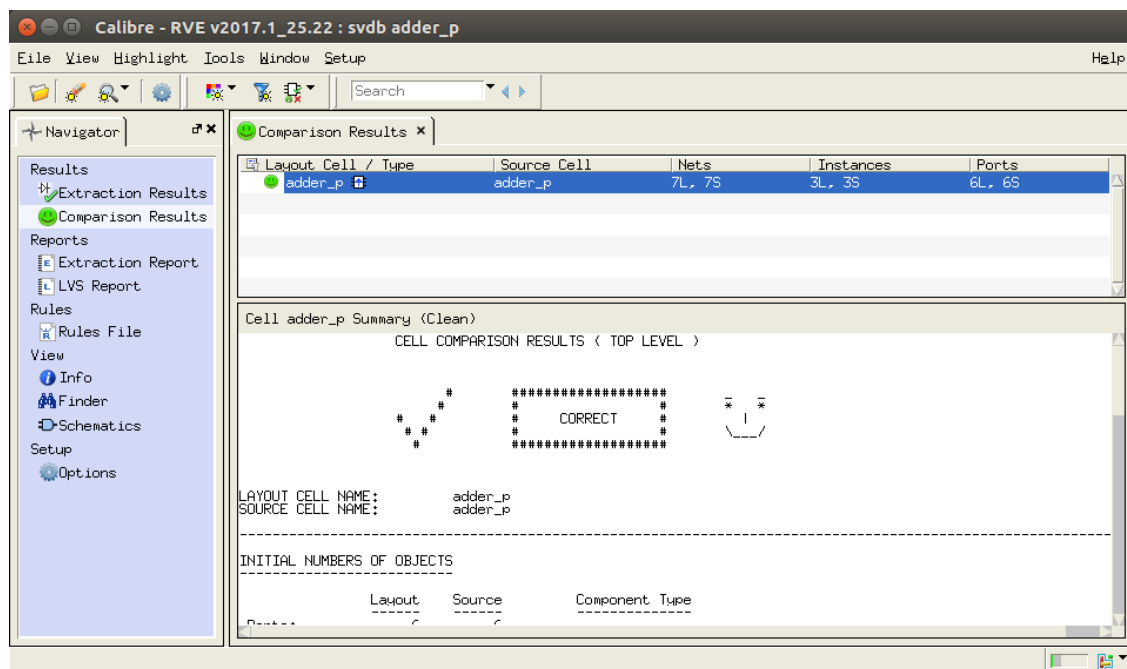

(a) LVS report

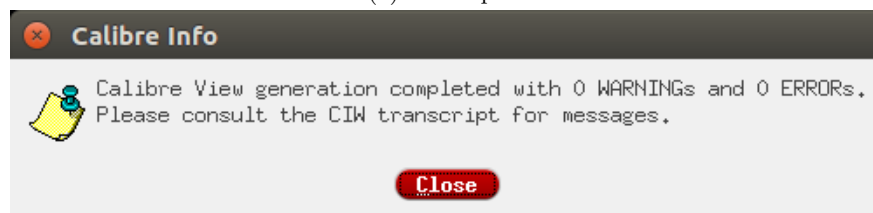

(b) PEX generation

Figure 5: Carry Generator

## Test Bench Simulation

For the following simulation, time period of clock and input signal is 1 ns.

## Generate

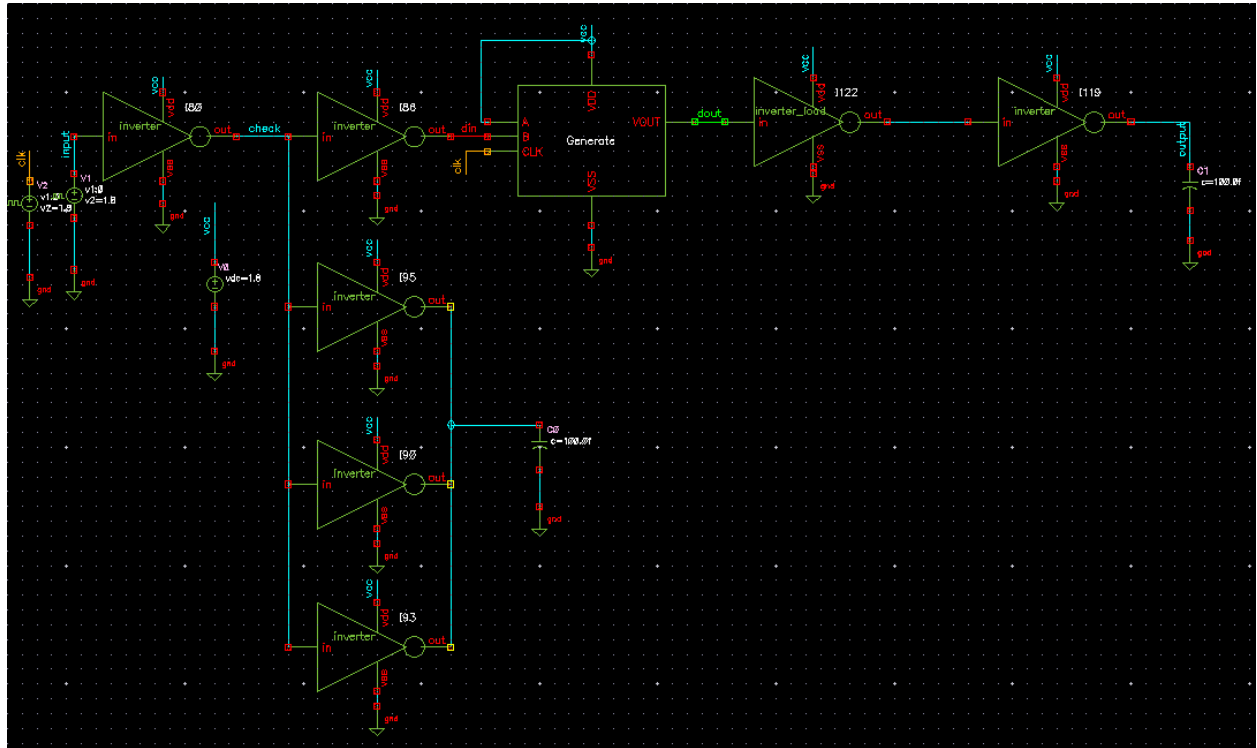


Figure 6: Generate

 


Figure 7: Generate

Table 2: Calculation of generate delay

Parameter	Value
Rise Time	141.339 <i>ps</i>
Fall Time	148.223 <i>ps</i>

## Propagate

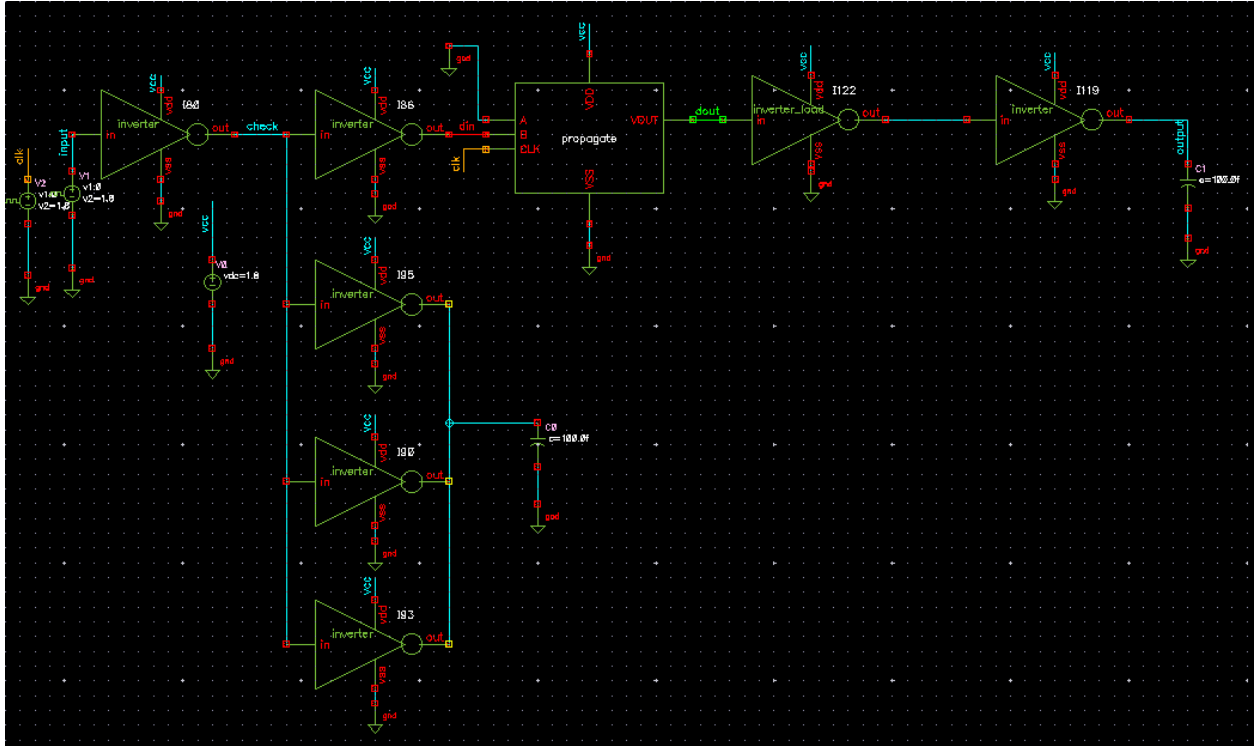


Figure 8: Test Bench

 


Figure 9: Delay

Table 3: Calculation of propagate delay

Parameter	Value
Rise Time	141.651 ps
Fall Time	145.575 ps



[illegible]

---

Page 9

Table 4: Calculation of carry delay

Parameter	Value
Rise Time	144.231 <i>ps</i>
Fall Time	150.529 <i>ps</i>

## VHDL Simulation

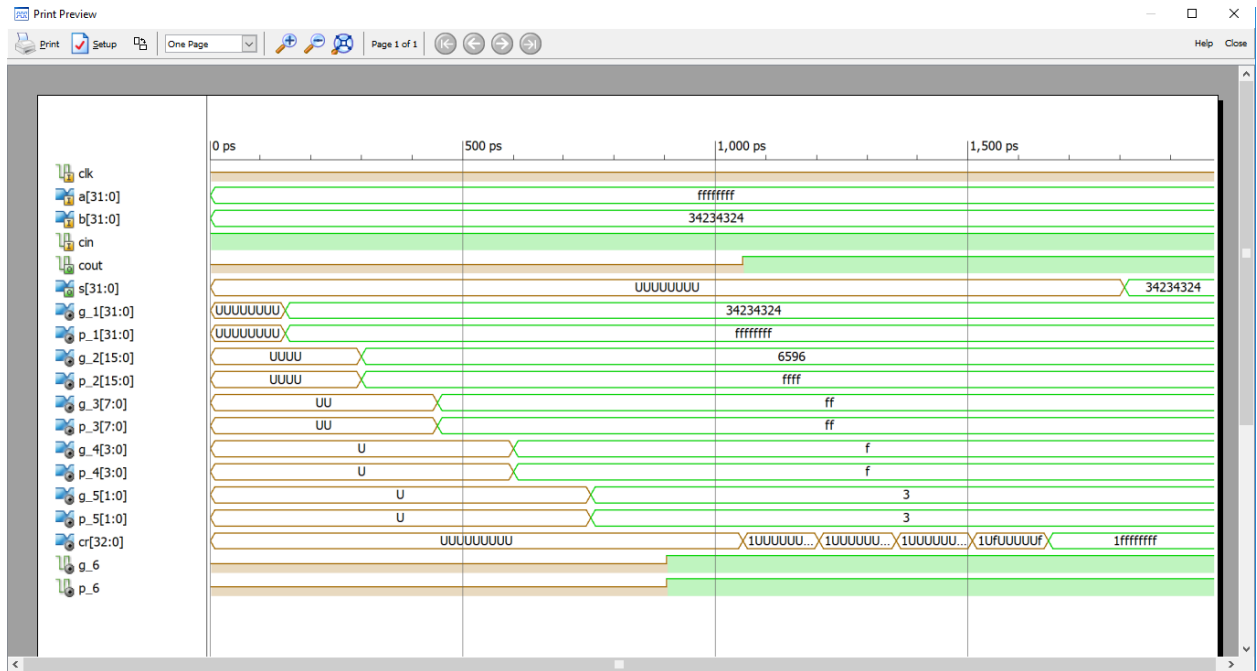


Figure 12: simulation Result

The clock frequency calculated is: 301.38 Mhz The maximum delay to generate the sum is 1659 ps.